


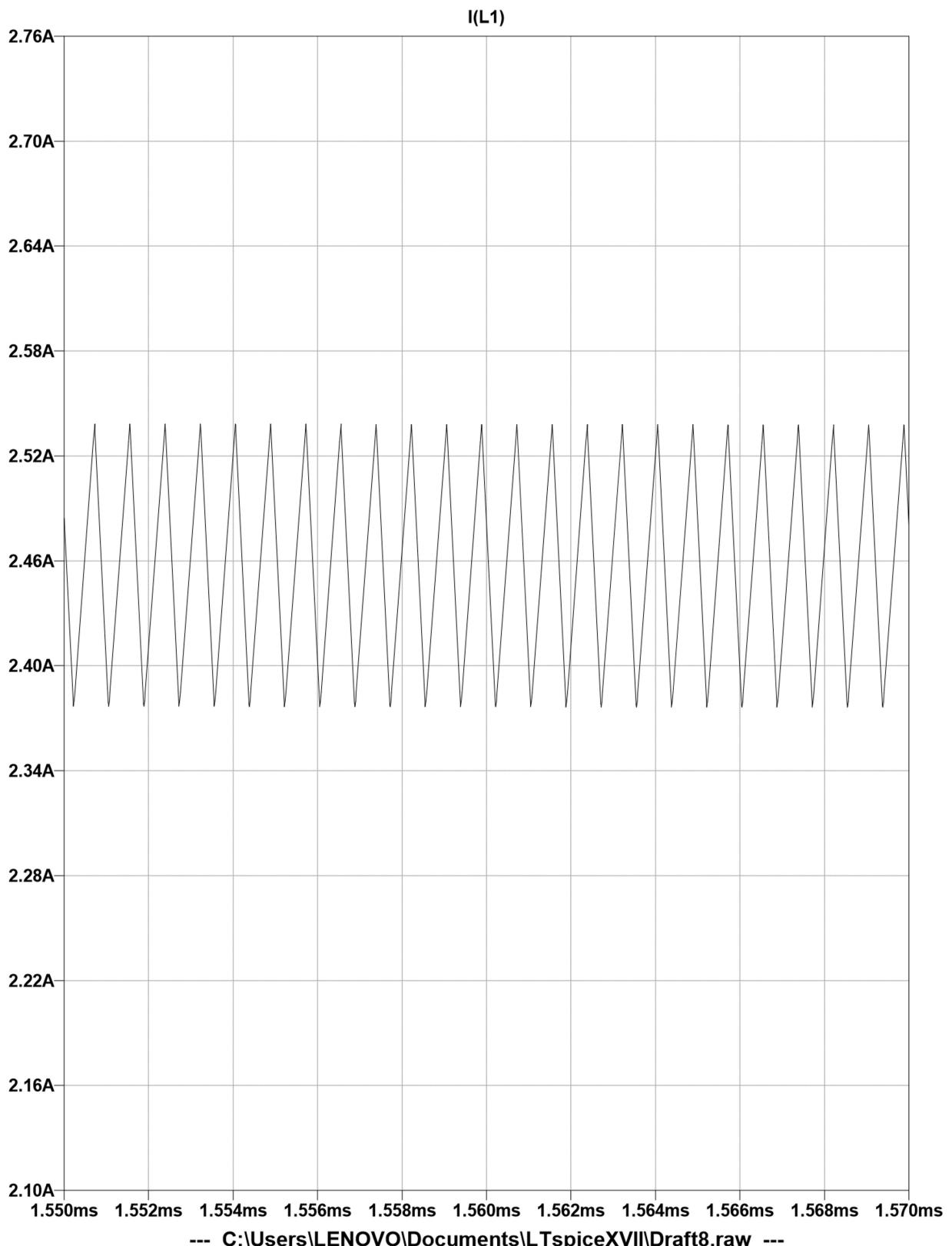



12 February 2020 16:04

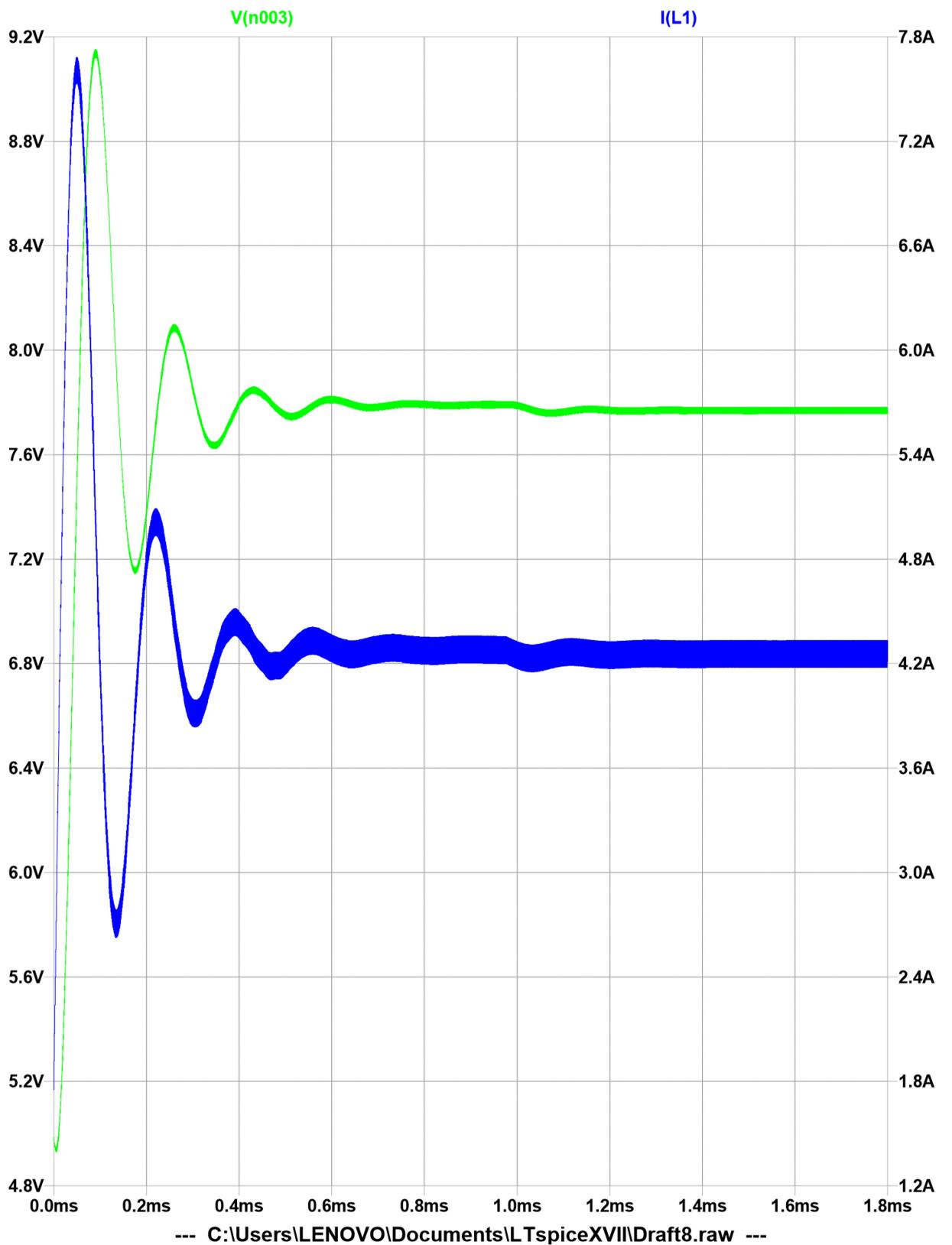

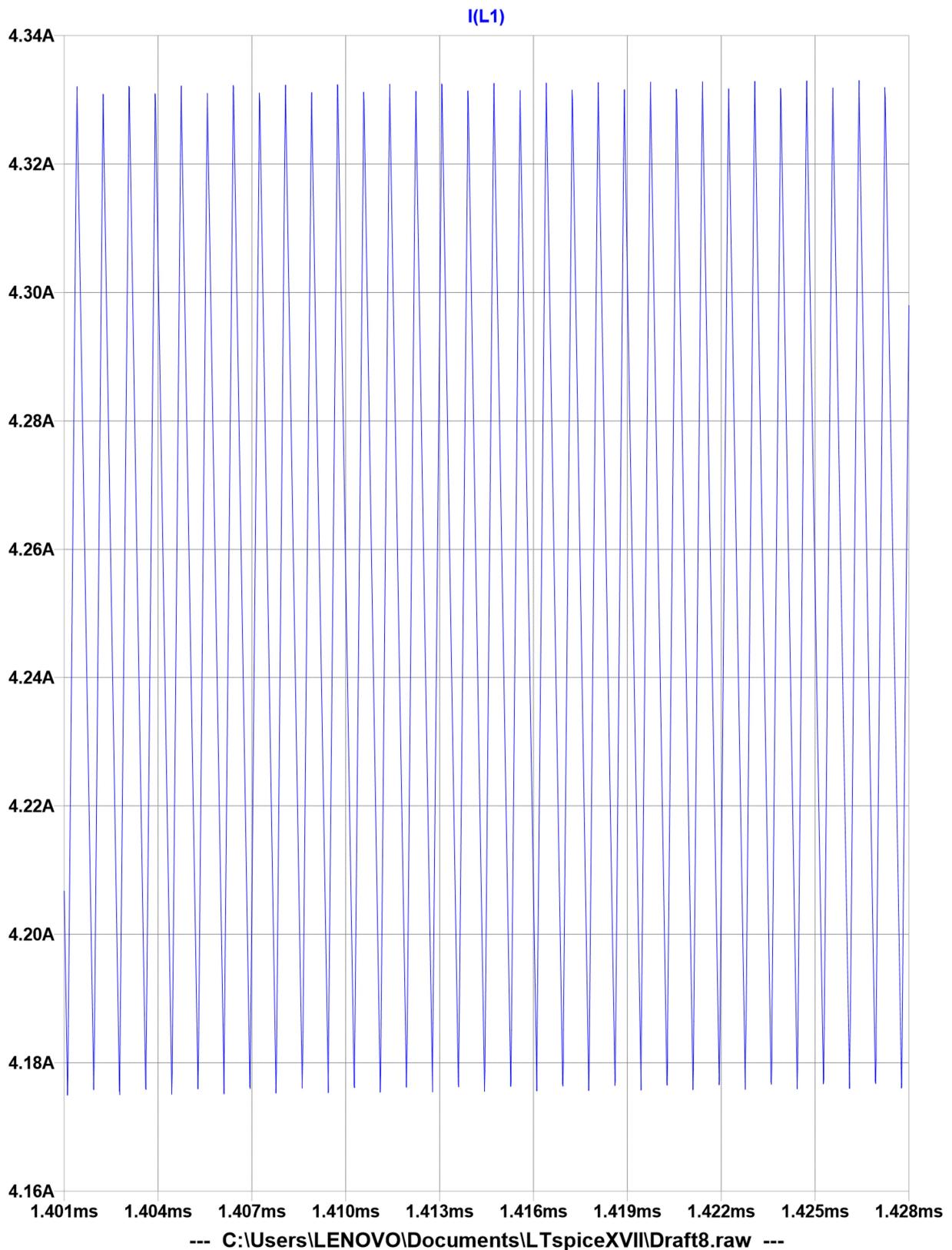

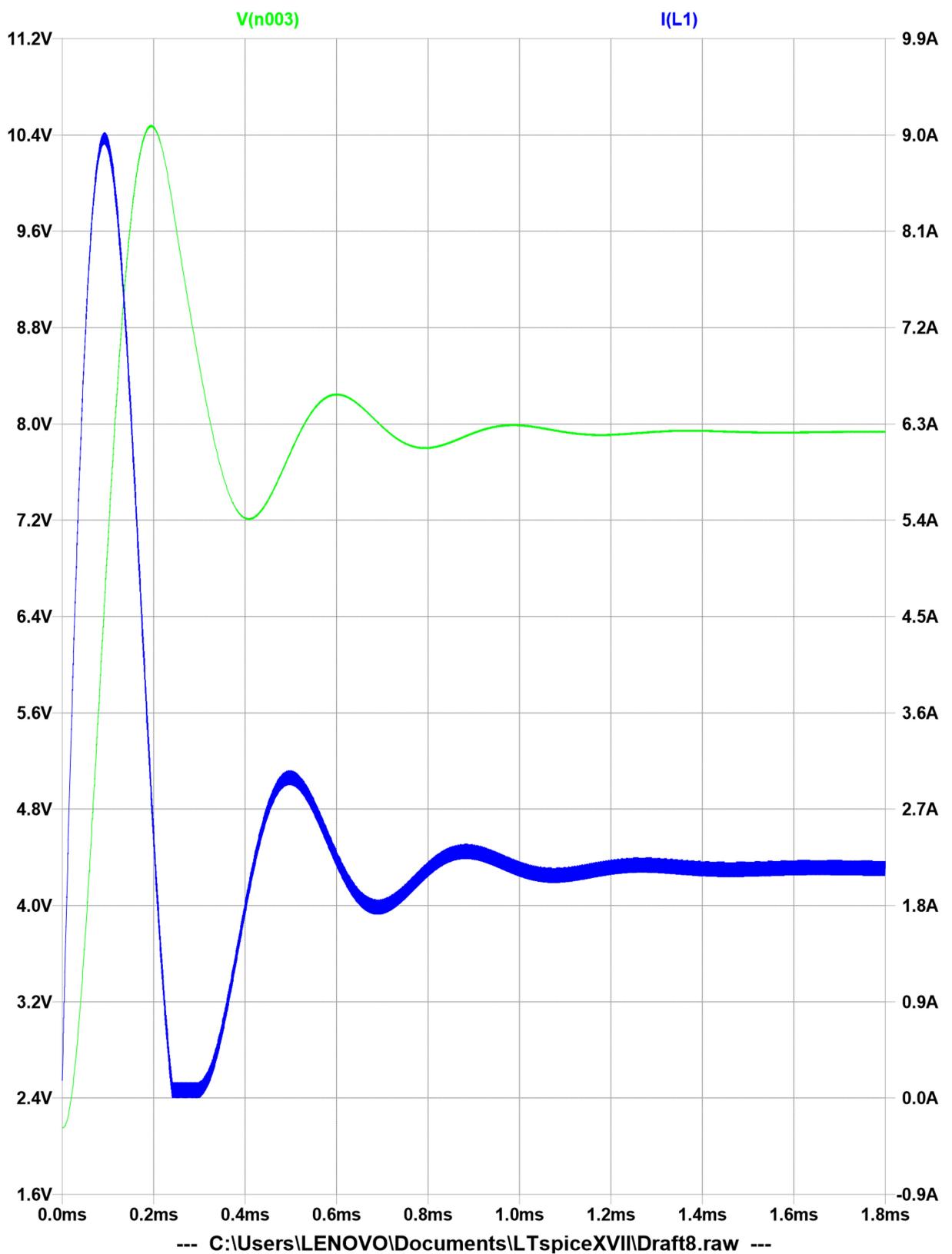




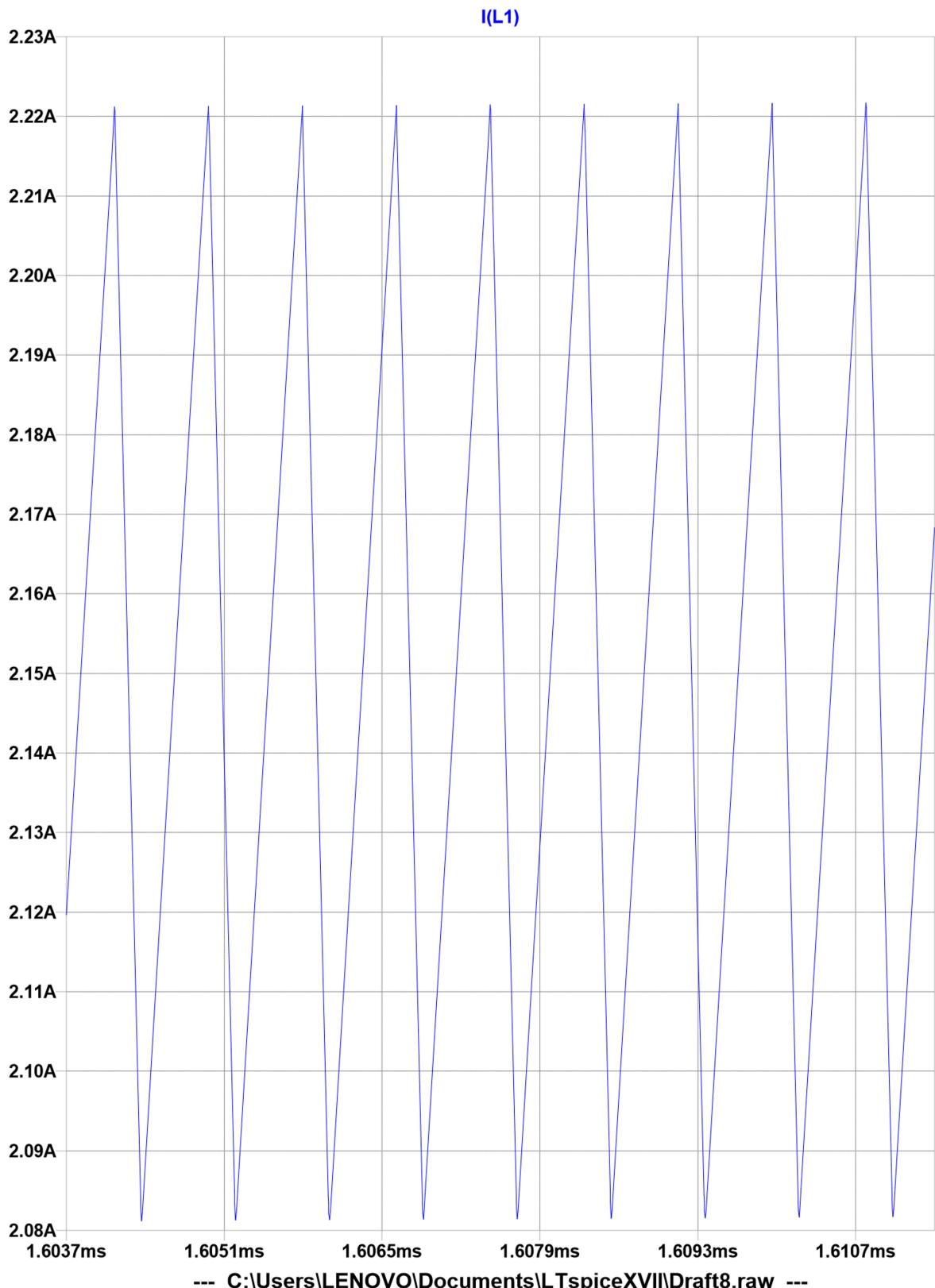

```

.tran 1.8m
.model SW SW(Vt = 1 Ron = 10m Roff = 1Meg )
.model dio D(Is=31.7u Rs= 0 N =1.5 mfg=OnSemi type=Schottky)

```

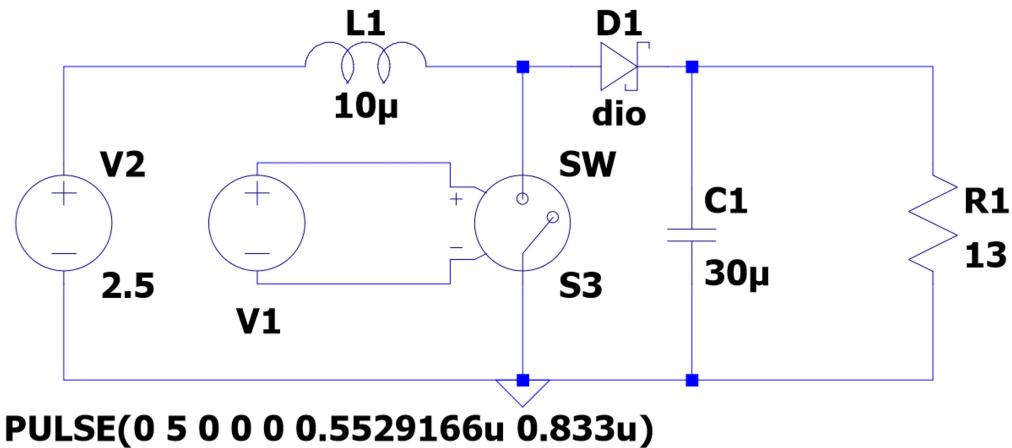


**PULSE(0 5 0 0 0 0.5529166u 0.833u)**

.tran 1.8m

.model SW SW(Vt = 1 Ron = 10m Roff = 1Meg )

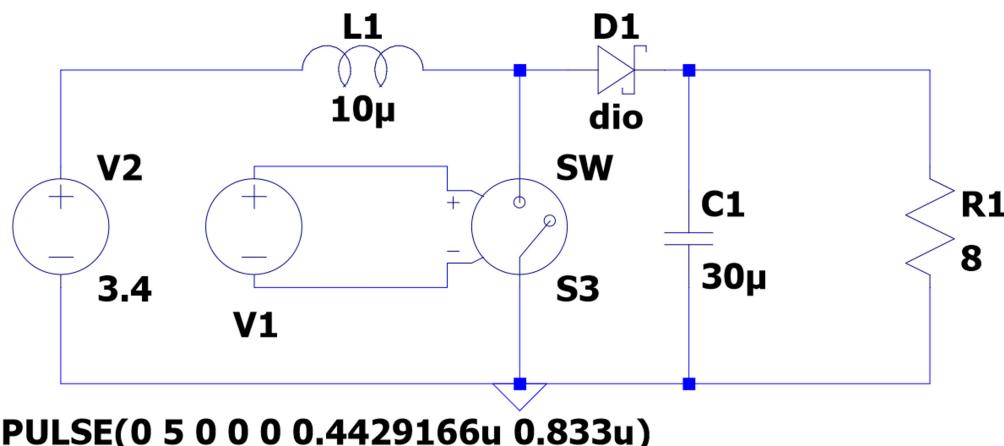
.model dio D(Is=31.7u Rs= 0 N =1.5 mfg=OnSemi type=Schottky)




**.tran 1.8m**

**.model SW SW(Vt = 1 Ron = 10m Roff = 1Meg )**

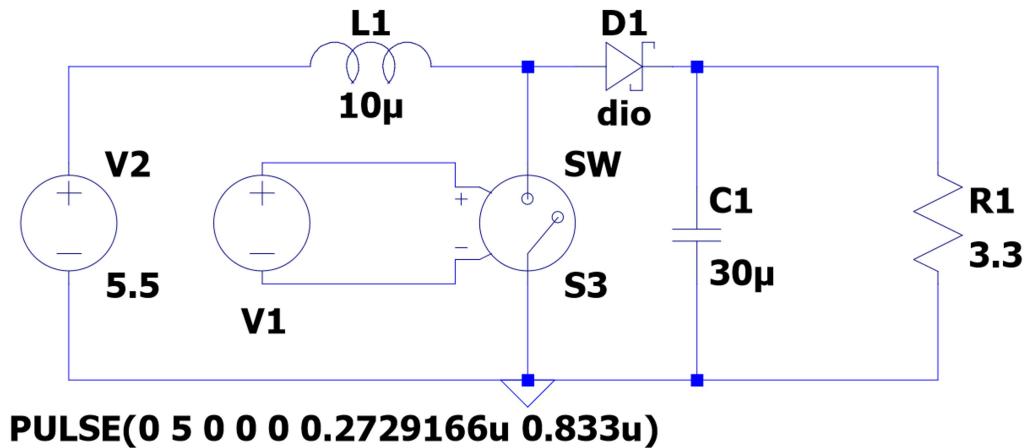**.model dio D(Is=31.7u Rs= 0 N =1.5 mfg=OnSemi type=Schottky)**



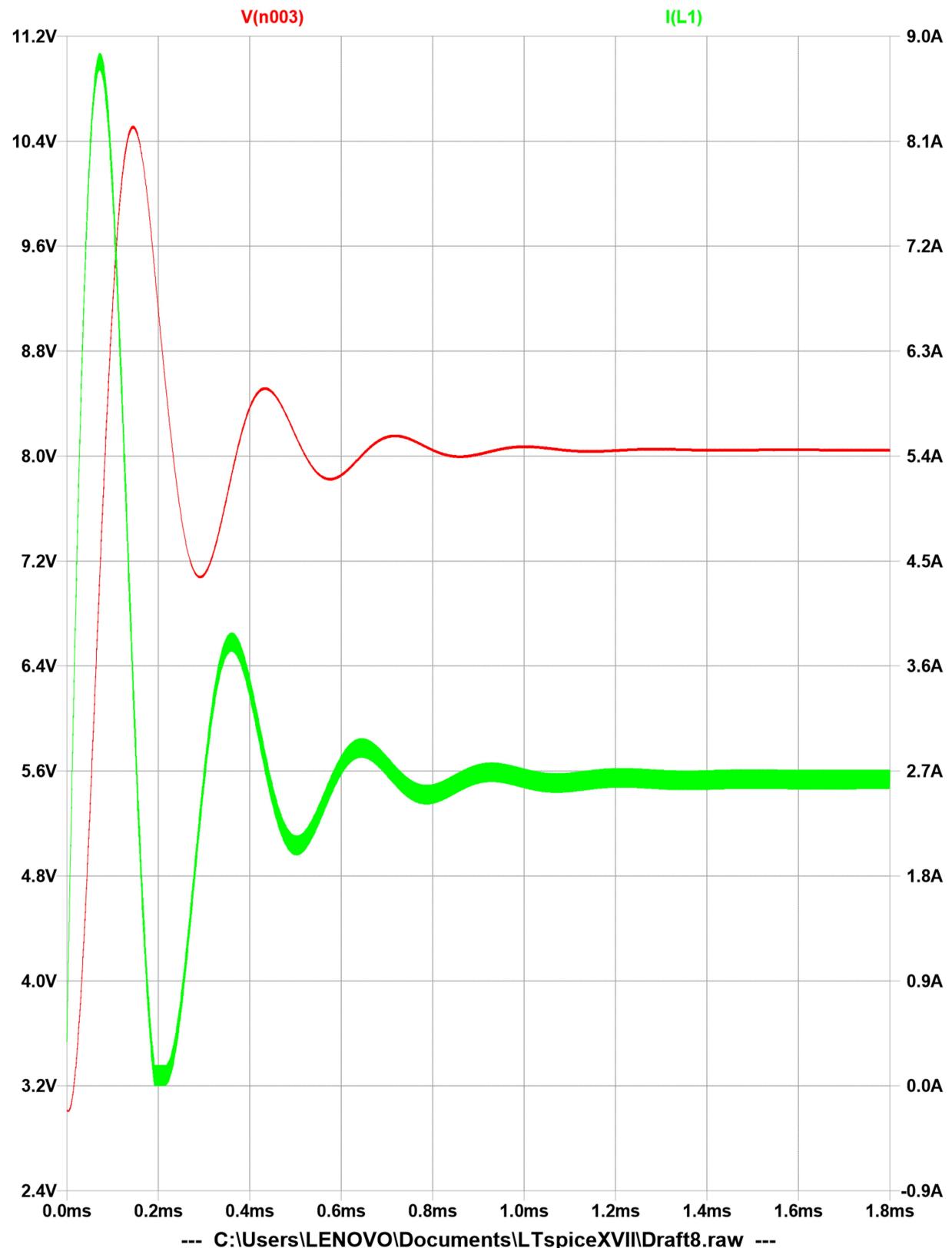

--- C:\Users\LENOVO\Documents\LTspiceXVII\Draft8.raw ---